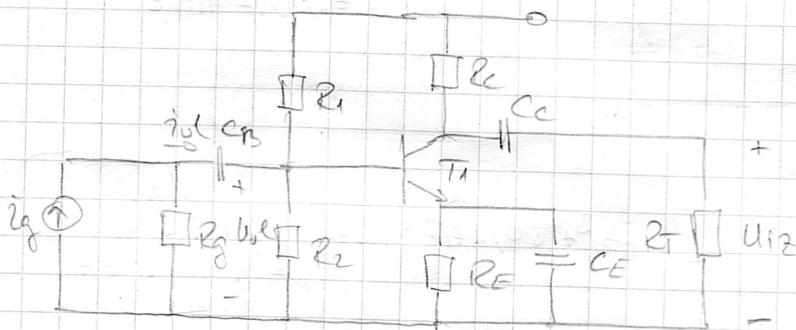


Zadanie 1.)

$$U_{CC} = 12V \quad R_1 = 50k\Omega \quad C_0 = 4\mu F \quad R_T = 200k\Omega \quad R_E = 50k\Omega \quad R_C = 4k\Omega$$

$$R_E = 500\Omega \quad C_E = 100\mu F \quad C_C = 5\mu F \quad R_T = 12\Omega \quad r_{bb} = 50\Omega \quad C_{be} = 50\text{pF}$$

$$A_{Ig} = ?$$




$$U_B = \frac{R_2 \cdot U_{CC}}{R_1 + R_2} = \frac{503 \cdot 12}{2002 + 503} = 2.4V \quad R_C = R_1 \| R_2 = 40k\Omega$$

$$I_B = \frac{U_B - U_T}{R_B + (1+\beta)R_E} = \frac{2.4 - 0.7}{403 + 12 \cdot 500} = 16.915\mu A \quad I_C = 2.03mA$$

$$U_{CE} = U_{CC} - I_C(R_C + R_E) = 12 - 2.03 \cdot 2^2 (4^2 + 500) = 2.86V$$
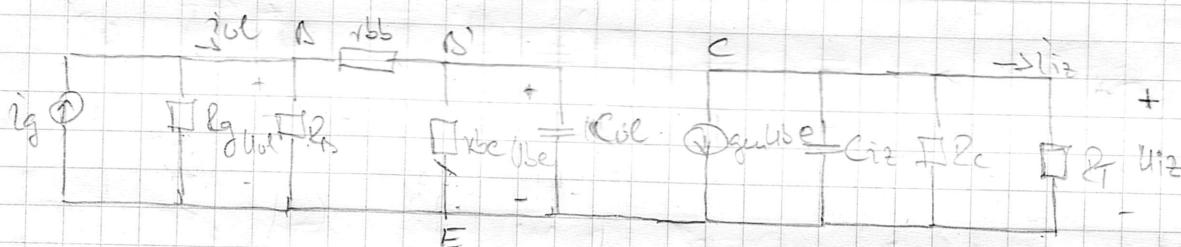
$$r_{be} = U_{be} = 1.478k\Omega \quad g_m = \frac{I_C}{U_{be}} = 81.194\mu A/V$$



$$A_{vo} = \frac{U_{iz} \cdot U_{be}}{U_{be} \cdot U_{il}}$$

$$\frac{U_{iz}}{U_{be}} = k = -g_m \cdot R_C \| R_T = -21.2^3 \cdot 4^{3/1/1^3} = -64.95$$

$$A_{vo} = -62.82$$

$$A_{Igo} = \frac{i_{iz}}{i_{be}} \cdot \frac{i_{be}}{i_g} = A_{vo} \cdot \frac{R_{UL}}{R_T} \cdot \frac{i_{ul}}{i_g}$$

$$P_{UL} = (R_S + r_{be} + b_L) = 403/(1.478^2 + 50) = 1.4747^2 k\Omega$$

$$\frac{i_{ul}}{i_g} = \frac{R_g}{R_{UL} + R_g} = \frac{503}{503 + 1.478^2} = 0.8414$$

$$A_{Igo} = -62.82 \cdot \frac{1.478^3}{1^3} \cdot 0.8414 = -89.87$$

$$C_{UL} = C_{be} + (b_L(1-\zeta)) = 247.85\text{pF}$$

$$(1-\zeta) = (b_L(\zeta-1)) / \zeta = 3.04\text{pF}$$

$$T_{U2} = C_{UL} \left[((R_g || R_S) + r_{bb}) || r_{be} \right] = 247.85^{-1} \left[((503 || 4^2) + 50) || 1.478^3 \right] = 843.52\text{ns}$$

$$\omega = 2.91 \cdot 10^6 \text{ rad/s}$$

$$f = 663.3 \text{ Hz}$$


$$T_{iz} = C_{iz} \left[R_C || R_T \right] = 3.04^{-1} \left[4^3 || 1^3 \right] = 2.432\text{ns} \quad \omega = 411.18 \cdot 10^6 \text{ rad/s} \quad f = 65.44 \text{ MHz}$$

$$f_g = 463.3 \text{ Hz}$$

Zadatok 2.

$$\begin{aligned}
 U_{cc} &= 15V \quad R_g = 500\Omega \quad C_B = 4\mu F \quad R_1 = 200\Omega \quad R_2 = 100\Omega \quad R_E = 400\Omega \\
 C_E &= 100\mu F \quad R_L = 2.5k\Omega \quad C_T = 300\mu F \quad r_e = 100 \quad r_{bb} = 50\Omega \quad C_{BE} = 40\mu F \\
 C_{BC} &= 1.2\mu F
 \end{aligned}$$

$$A_{v2} = ?$$

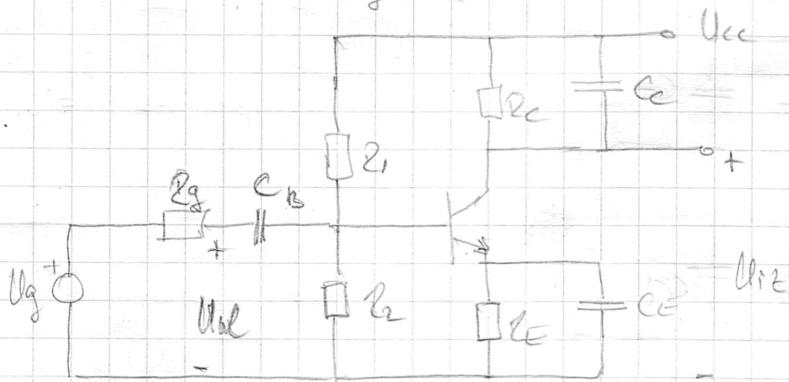

$$U_B = \frac{R_2 \cdot U_{cc}}{R_1 + R_2} = \frac{100^3 \cdot 15}{200^3 + 100^3} = 5V$$


$$R_B = R_1 \| R_2 = 100^3 \| 200^3 = 66.6\Omega$$

$$I_C = \frac{U_B - U_T}{R_B + (1+\beta)R_E} = \frac{5 - 0.7}{66.6^3 + 101 \cdot 400} = 40.18\mu A \quad I_C = 40.18\mu A$$

$$r_{be} = 622.09 \Omega$$

$$g_m = \frac{I_C}{U_{th}} = 160.74 \mu A/V$$
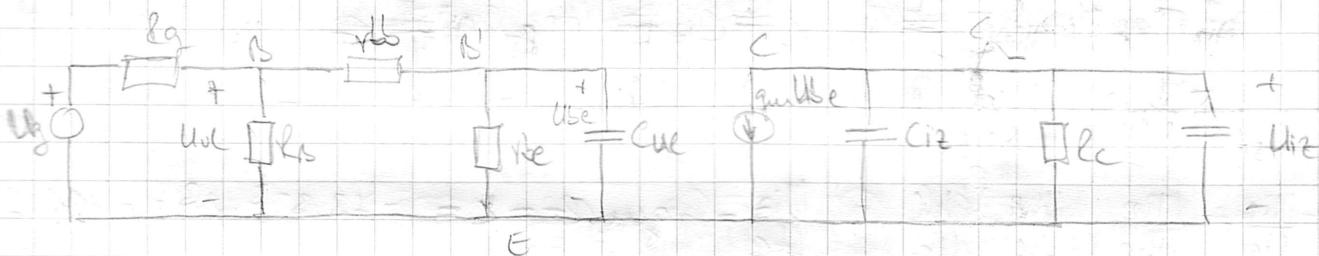
$$\begin{aligned}
 U_{CE} &= U_{cc} - I_C(R_L + R_E) \\
 &= 3.345V
 \end{aligned}$$



$$A_{v2} = \frac{U_{v2}}{U_{v1}} = \frac{U_{v2}}{U_{BE}} \cdot \frac{U_{BE}}{U_{v1}}$$

$$\frac{U_{v2}}{U_{BE}} = -g_m R_C \stackrel{k}{=} -160 \cdot 74^{-3} \cdot 2.5 = -401.85$$

$$\frac{U_{BE}}{U_{v1}} = \frac{r_{be}}{r_{bb} + r_{be}} = \frac{622.09}{622.09 + 50} = 0.9256$$

$$\begin{aligned}
 R_{UL} &= R_C \| (r_{bb} + r_{be}) \\
 &= 66.6^2 \| (50 + 622.09) \\
 &= 665.37 \Omega
 \end{aligned}$$

$$\frac{U_{v1}}{U_g} = \frac{R_{UL}}{R_g + R_{UL}} = \frac{665.37}{500 + 665.37} = 0.5709$$

$$A_{v2} = -212.36$$

$$C_{UL} = C_{BE} + C_{BC}(1-k) = 523.42 \mu F$$

$$C_{T2} = C_{BE} \left(\frac{k-1}{k} \right) + C_E = 1.203 \mu F + 300^{-12} = 301.203 \mu F$$

$$Z_{UL} = C_{UL} \left[(R_g \| R_{UL}) + r_{bb} \right] \| C_{T2} = 523.42^{-12} \left[(500 \| 66.6^2) + 50 \right] \| 622.09 = 152.2448 \Omega$$

$$\omega = 6.568 \cdot 10^6 \text{ rad/s}$$

$$f_{T2} = C_{T2} \left[2\pi \right] = 301.203^{-12} \cdot 2 \cdot \pi^3 = 753 \text{ Hz} \quad \omega = 1.328 \cdot 10^6 \text{ rad/s}$$

$$f = 211.36 \text{ Hz}$$

$$f_g = 211.36 \text{ Hz}$$


Zadanie 2)

$$U_{DD} = 15V \quad R_g = 1k\Omega \quad C_{ox} = 500\text{pF} \quad R_L = 2\text{k}\Omega \quad R_o = 48\text{k}\Omega$$

$$R_s = 500\Omega \quad C_s = 20\text{pF} \quad C_0 = 1\text{nF} \quad R_T = 6\text{k}\Omega \quad I_{DSS} = 8\text{mA} \quad V_p = -2V$$

$$C_{gs} = 3\text{pF} \quad C_{gd} = 2\text{pF}$$

$$A_{vg} = ?$$

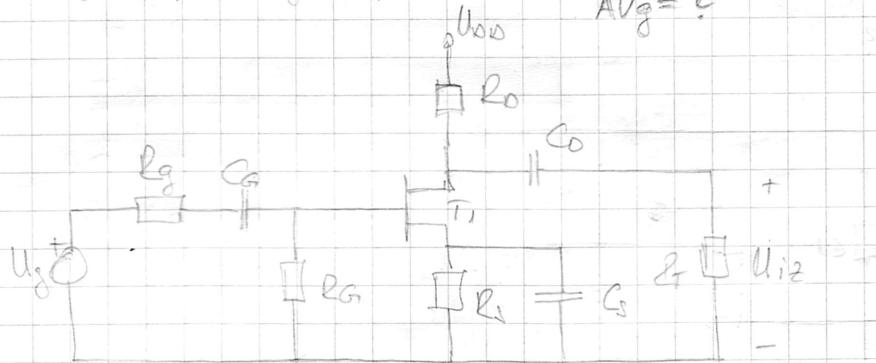

$$0 = U_{g1} + I_D R_s$$

$$I_D = I_{DSS} \left(1 - \frac{U_{g1}}{U_p} \right)^2$$

$$-U_{g2} = I_{DSS} + 2I_{DSS} \frac{U_{g2}}{U_p} + I_{DSS} \frac{U_{g2}}{U_p^2}$$


$$U_{g2}^2 \left(\frac{I_{DSS}}{U_p} \right) + U_{g2} \left(\frac{1}{R_s} - 2 \frac{I_{DSS}}{U_p} \right) + I_{DSS} = 0 \quad U_{g2}^2 \left(\frac{2}{4} \cdot 10^{-3} \right) + U_{g2} \left(\frac{1}{500} + \frac{16}{2} \cdot 10^{-3} \right) + 8 \cdot 10^{-3} = 0$$

$$U_{g2}^2 (2 \cdot 10^{-3}) + U_{g2} (10^{-3}) + 8 \cdot 10^{-3} = 0 \quad U_{g2}^2 + U_{g2} (5 \cdot 10^{-3}) + 4 \cdot 10^{-3} = 0 \quad U_{g2,1,2} = \frac{-5 \pm \sqrt{25 + 32}}{2}$$

$$U_{g2} = -1V \quad I_D = \frac{1}{500} = 2\text{mA}$$

$$U_{DS} = U_{DD} - I_D (R_o + R_s) = 15 - 2 \cdot 2 (48 + 500) = 6V$$
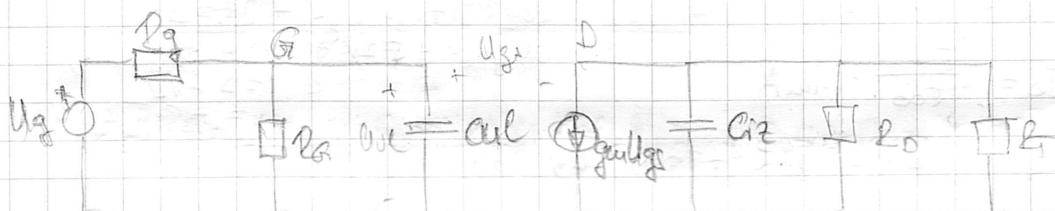
$$g_m = 2I_{DSS} \left(1 - \frac{U_{g2}}{U_p} \right) = 4\text{mA/V}$$



$$A_{vg} = \frac{U_{d2}}{U_{g1}} = \frac{U_{d2}}{U_{g1}} \cdot \frac{U_{g2}}{U_{g2}} \cdot \frac{U_{g2}}{U_{g2}} \cdot \frac{U_{d2}}{U_{g2}}$$

$$\frac{U_{d2}}{U_{g2}} = -g_m R_o / R_T = k = -4 \cdot 10^{-3} \cdot 48 / 6 = -3.2$$

$$A_{vg} = -3.2 \cdot 10^{-3} \approx -3.6$$

$$\frac{U_{d2}}{U_{g2}} = \frac{U_{g2}}{U_{g2}} = 1$$

$$\frac{U_{d2}}{U_{g2}} = \frac{2q}{R_s + R_g} = \frac{2 \cdot 10^{-6}}{13 + 76} = 0.143$$

$$C_{UL} = C_{gs} + C_{gd} (1 - k) = 24.2 \text{ pF} \quad C_{d2} = C_{gd} \left(\frac{k-1}{k} \right) = 2.2 \text{ pF}$$

$$T_{UL} = C_{UL} (R_s // R_g) = 24.188 \text{ ns} \quad \omega = 41.24 \cdot 10^6 \text{ rad/s} \quad f = 6.58 \text{ MHz}$$

$$T_{d2} = C_{d2} (R_o // R_T) = 5.128 \text{ ns} \quad \omega = 189.4 \cdot 10^6 \text{ rad/s} \quad f = 30.143 \text{ MHz}$$


$$f_g = 6.58 \text{ MHz}$$

Zadatak 4

$$U_{DD} = 15V \quad R_g = 12\Omega \quad C_G = 50pF \quad R_G = 1M\Omega \quad L_T = 2,5\mu H \quad L_S = 400nH$$

$$C_T = 50pF \quad C_S = 20pF \quad I_{DSS} = 15mA \quad U_P = -3V \quad C_{GS} = 1,5pF \quad C_{GD} = 1,5pF$$


$$A_V = 2$$

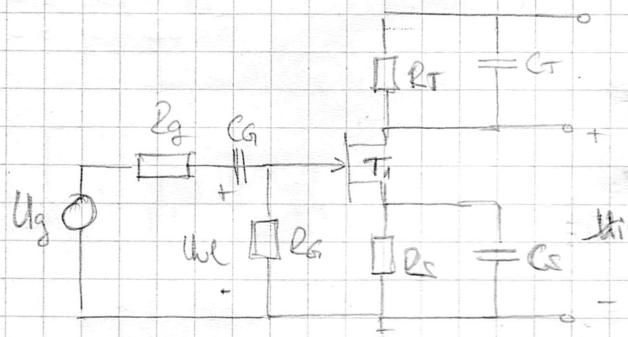

$$0 = U_{GS} + I_D R_S \quad I_D = I_{DSS} \left(1 - \frac{U_{GS}}{U_P}\right)^2 \quad U_{GS}^2 \left(\frac{I_{DSS}}{U_P^2}\right) + U_{GS} \left(\frac{1}{R_S} - \frac{2I_{DSS}}{U_P^2}\right) + I_{DSS} = 0$$

$$U_{GS}^2 \left(\frac{1}{15}\right) + U_{GS} \left(\frac{1}{400} + \frac{30^{-3}}{3}\right) + 15^{-3} = 0 \quad U_{GS}^2 (1) + U_{GS} (7,5) + 9 = 0$$
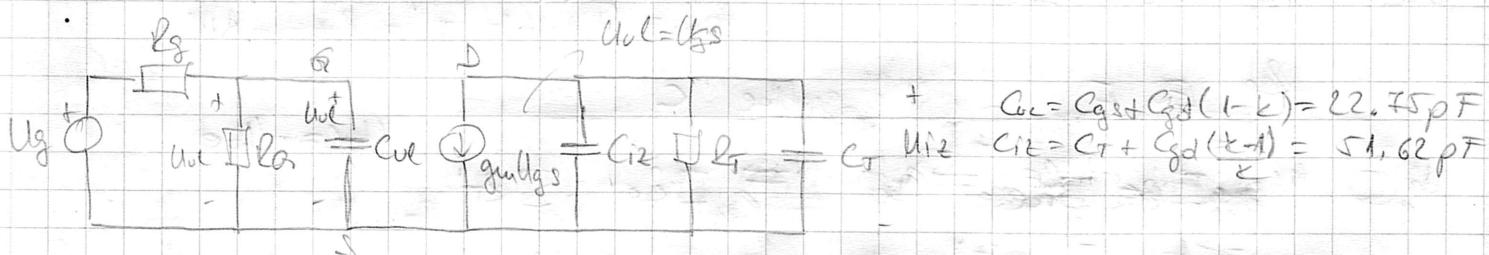
$$I_D = \frac{1,5}{400} = 3,75mA \quad g_m = -2 \frac{I_{DSS}}{U_P} \left(1 - \frac{U_{GS}}{U_P}\right) = 5mA/V \quad U_{GS1,2} = \frac{-7,5 \pm 4,5}{2} = -6 \quad (U_{GS} = -1,5)$$



$$A_V = \frac{U_{DZ}}{U_{DL}} = \frac{U_{DZ} \cdot U_{GS}}{U_{GS} + U_{DL}} \Rightarrow \frac{U_{DZ}}{U_{GS}} = -g_m R_T = -5 \cdot 2,5^3 = -12,5 \Rightarrow k = -12,5$$

$$\frac{U_{GS}}{U_{DL}} = 1 \quad A_V = -12,5$$

$$T_{DL} = C_{DL} (0) = 0 \quad \omega = \omega_0 \quad T_{DZ} = C_{DZ} [R_T] = 123,05 \mu s \quad \omega = 7,75 \cdot 10^6 \text{ rad/s}$$


$$f = 1,23 \text{ MHz}$$

$$f_g = 1,23 \text{ MHz}$$

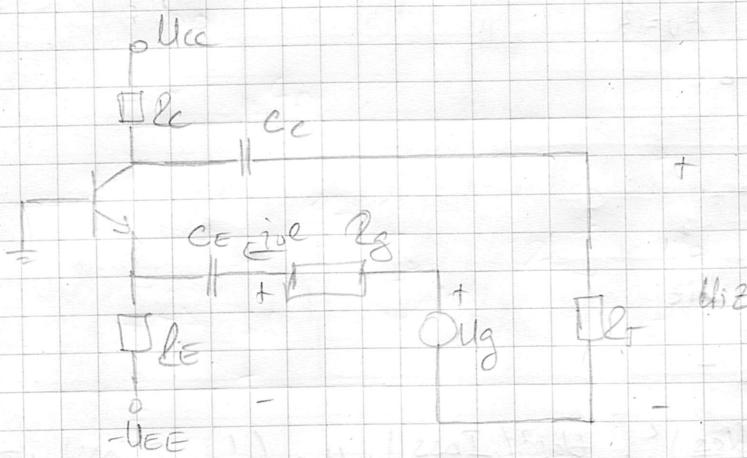Zadatak 5.

$$U_{CC} = U_{EE} = 12V \quad R_g = 50\Omega \quad C_E = 150\text{pF} \quad R_E = 4.8\Omega \quad R_C = 22\Omega$$

$$C_C = 2\mu\text{F} \quad Z = 3\Omega \quad \beta = 100 \quad C_{SE} = 50\text{pF} \quad C_{CE} = 3\text{pF} \quad V_{bb} = 0 \quad A_{v2} = ?$$




$$D = U_g + I_S(1 + \beta)R_E - U_{EE}$$

$$I_D = \frac{U_{EE} - U_T}{(1 + \beta)R_E} = \frac{12 - 0.7}{101 \cdot 4.8} = 27.93\text{nA} \quad I_C = 2.797 \text{ mA}$$

$$g_m = \frac{I_C}{U_{BE}} = 111.88 \text{ mAV} \quad r_{be} = 293.8 \Omega$$
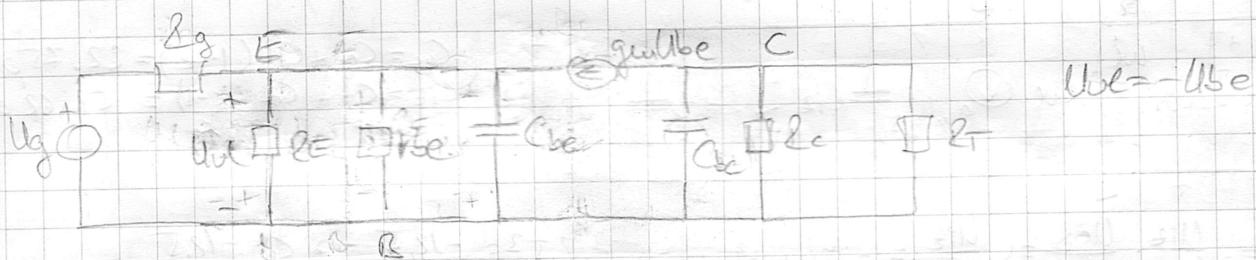
$$U_{CE} = U_{CC} + U_{EE} - I_C(R_C + R_E) = 24 - 2.797 \cdot (23 + 4.8) = 4.218 \text{ V}$$



$$A_{v2} = \frac{U_{in}}{U_{in}} = \frac{U_{in}}{U_{BE}} \cdot \frac{U_{BE}}{U_{in}} \cdot \frac{U_{in}}{U_{in}} \quad U_{in} = -g_{me} R_{in} R_L = -134.25$$

$$A_{v2} = 134.25$$

$$\frac{U_{BE}}{U_{in}} = \frac{U_{BE}}{-U_{BE}} = 1$$

$$\frac{U_{in}}{U_g} = \frac{R_{in}}{R_{in} + R_g}$$

$$R_{in} = R_E \parallel \frac{r_{be}}{1 + \beta} = 4.31 \parallel \frac{293.8}{101} = 8.83 \Omega$$

$$= \frac{8.83}{8.83 + 50} = 150 \cdot 1 \cdot 10^{-3} \Rightarrow A_{v2} = 134.25 \cdot 150 \cdot 10^{-3} = 20.15$$

$$Z_{in} = C_{BE} \cdot \left[R_g \parallel R_E \parallel \frac{r_{be}}{1 + \beta} \right] = 50^{-1} \left[(50 \parallel 4.8) \parallel 8.83 \right] = 375.25 \text{ pS} \quad \omega = 2.66 \text{ rad/s}$$

$$f = 421.13 \text{ MHz}$$

$$Z_{in} = C_{BE} \left[R_C \parallel R_T \right] = 3^{-1} \left[2^3 \parallel 3^3 \right] = 3.6 \text{ nS} \quad \omega = 277.7 \cdot 10^6 \text{ rad/s}$$


$$f = 44.21 \text{ MHz}$$

$$f_2 = 44.21 \text{ MHz}$$

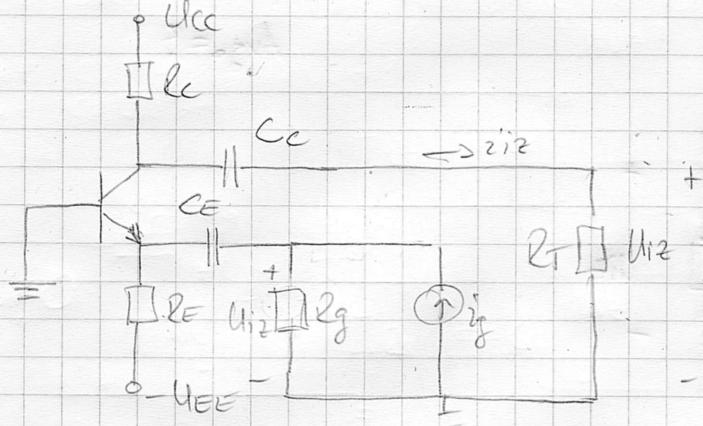Zadatak 6.

$$U_{CC} = U_{EE} = 10V \quad R_g = 5k\Omega \quad C_E = 120\mu F \quad R_E = 5k\Omega \quad R_C = 4k\Omega$$

$$C_C = 1.5\mu F \quad R_T = 1.5k\Omega \quad f_s = 150 \quad C_{SE} = 40\mu F \quad C_{CE} = 3\mu F \quad A_{ig} = ?$$




$$\bar{U} = U_f - U_{EE} + I_D (1 + \beta) R_E \quad I_C = \frac{U_{EE} - U_f}{(1 + \beta) R_E} = \frac{10 - 0.7}{151 \cdot 53} = 12.318 \mu A$$

$$r_{be} = 2.03 k\Omega$$

$$I_C = 1.847 \text{ mA} \quad g_m = 73.91 \text{ mA/V}$$
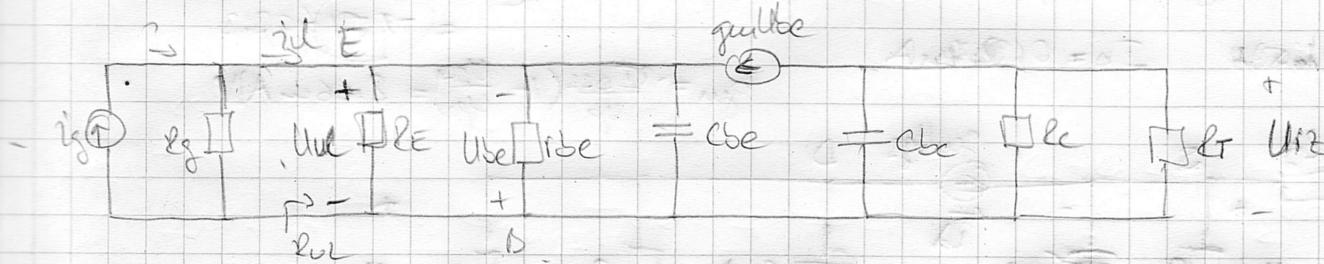
$$U_{CE} = U_{CC} + U_{EE} + I_C (R_C + R_E) = 20 - 1.847 \cdot 2 (53 + 53) = 3.377 V$$



$$A_V = \frac{U_{i2}}{U_{be}} = \frac{U_{i2}}{U_{be}} \frac{U_{be}}{U_{ce}}$$

$$U_{i2} = -g_m R_C \| R_T = -73.91 \cdot 43 \| 1.53 = -80.63$$

$$\frac{U_{be}}{U_{ce}} = -1 \quad A_V = 80.63$$

$$A_{ig} = \frac{U_{i2}}{U_{be}} \cdot \frac{U_{ce}}{U_{ig}} = \frac{U_{i2}}{U_{ig}} = A_V \cdot \frac{R_{UL}}{R_T}$$

$$\frac{R_{UL}}{R_T} = 0.720$$

$$R_{UL} = R_E \| \frac{r_{be}}{1 + \beta} = 53 \| \frac{2.03^2}{151} = 13.4 \Omega$$

$$L_{i2} = C_{be} [R_E \| R_T] \parallel \frac{r_{be}}{151} = 584.87 \mu s; \omega = 1.87 \cdot 10^3 \text{ rad/s} \quad f = 297.5 \text{ MHz}$$


$$L_{i2} = C_{bc} [R_C \| R_T] = 3.27 \text{ nH} \quad \omega = 305.5 \cdot 10^6 \text{ rad/s} \quad f = 48.63 \text{ MHz}$$

$$f_g = 48.63 \text{ MHz}$$

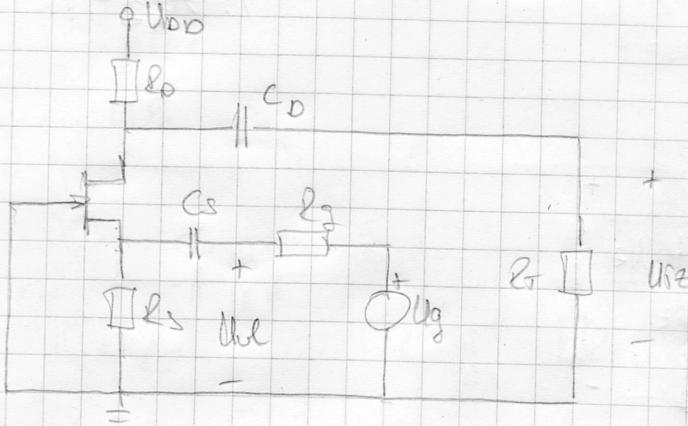Zadanie 7.

$$U_{DD} = 20V \quad R_g = 500 \quad C_s = 50\mu F \quad R_s = 700\Omega \quad R_D = 62\Omega$$

$$C_0 = 5\mu F \quad R_T = 10k\Omega \quad I_{DSS} = 8mA \quad U_p = -3V \quad C_{gs} = 3\mu F \quad C_{gd} = 2\mu F$$



$$A_{Vg0} = ?$$

$$0 = U_{bg} + I_D R_s \quad I_D = I_{DSS} \left(1 - \frac{U_{bg}}{U_p} \right)^n$$

$$U_{gs}^2 \left(\frac{I_{DSS}}{U_p^n} \right) + U_{gs} \left(\frac{1}{R_s} - \frac{2I_{DSS}}{U_p} \right) + I_{DSS} = 0 \quad U_{gs} \left(\frac{8}{3} \right) + U_{gs} \left(\frac{1}{700} + \frac{16}{3} \right) + 8 = 0$$


$$U_{gs}^2 (1) + U_{gs} \left(\frac{1}{700} \right) + 8 = 0$$

$$U_{gs} = -1.5V \quad I_D = 0.2mA$$

$$U_{gs1,2} = \frac{-1.5 \pm 4.5}{2} = -6$$

$$= -1.5V$$
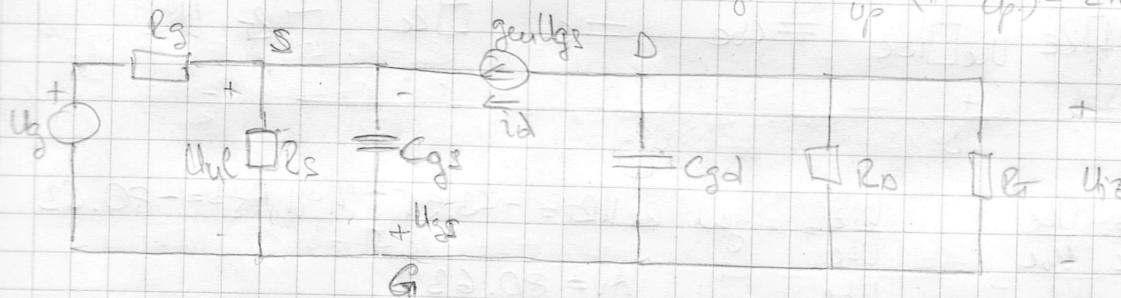
$$g_{mi} = -\frac{2I_{DSS}}{U_p} \left(1 - \frac{U_{gs}}{U_p} \right) = 2.66mA/V$$



$$A_{Vg} = \frac{U_{DZ}}{U_{bg}} = \frac{U_{DZ}}{U_{gs}} \cdot \frac{U_{gs}}{U_{el}} \cdot \frac{U_{el}}{U_g}$$

$$U_{DZ} = -g_{mi} R_D / R_T = -3.375$$

$$Z_{UL} = R_S \parallel \frac{1}{g_{mi}} = 250.4\Omega$$

$$\frac{U_{gs}}{U_{el}} = -1$$

$$\frac{U_{el}}{U_g} = \frac{R_{el}}{R_g + Z_{UL}} = 0.333$$

$$A_{Vg} = 3.328$$

$$Z_{UL} = C_{gs} \left[(R_g \parallel R_S) \parallel \frac{1}{g_{mi}} \right] = 500.55\Omega \quad \omega = 1.997 \cdot 10^9 \text{ rad/s} \quad f = 317.36 \text{ MHz}$$

$$T_{12} = C_{gd} [R_D \parallel R_T] = 7.5 \text{ ns} \quad \omega = 133.3 \cdot 10^6 \text{ rad/s} \quad f = 21.22 \text{ MHz}$$

$$f_g = 21.22 \text{ MHz}$$